



ITESO

**Universidad Jesuita
de Guadalajara**

Design and simulation of a pipeline processor based on the MIPS architecture

Raúl Méndez Álvarez

7/19/19

Arquitectura Computacional

Rodrigo Aldana López


Repository: <https://github.com/RaulMendezA/Practica-3---AC>

1 – Design changes and process:

For the pipeline, I first had to create some sort of internal language or system in order to name each of the new components for each pipeline. For example: ID_Instruction_wire_EX, both for entries and exits, in this way it is easier to realize where exactly is a certain cable; basically, all of the new component had the cable or module type in the middle and its connecting components on both sides.

I also made the decision to only pass the fundamental cables through the pipeline so that the forward unit could work. For this, the diagram provided in the presentation "Digital design with verilog HDL" was followed since using a different approach would be a bit confusing.

Pipelined Control

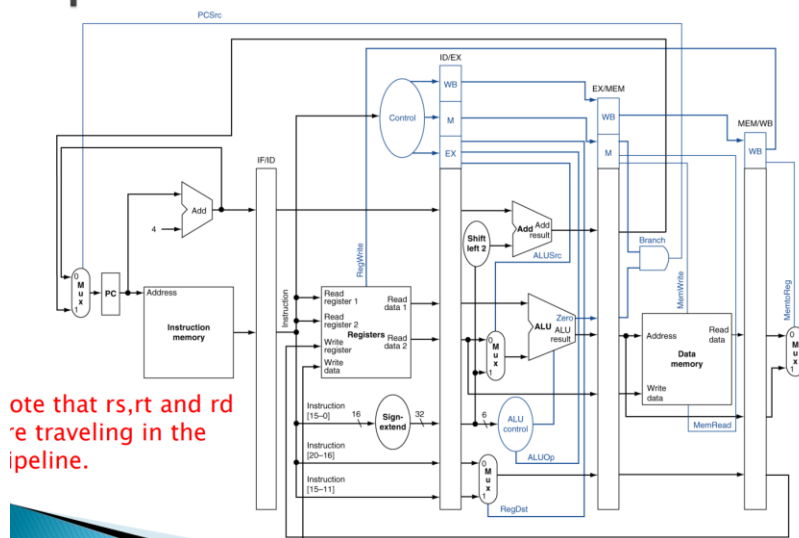

In order to begin migrating my original single-cycle model to a pipelined/multi-cycle approach, I had to change the register from posedge to negedge:

```
module Register
#(
    parameter N=32
)
(
    input clk,
    input reset,
    input enable,
    input  [N-1:0] DataInput,

    output reg [N-1:0] DataOutput
);
always@(negedge reset or negedge clk) begin
    if(reset==0)
        DataOutput <= 0;
    else
        if(enable==1)
            DataOutput<=DataInput;
end
end
```

Whereas the new pipeline module created would then be updating on posedge:

```
module Pipeline
#(
    parameter N=32
)
(
    input clk,
    input reset,
    input enable,
    input  [N-1:0] DataInput,

    output reg [N-1:0] DataOutput
);
always@(negedge reset or posedge clk) begin
    if(reset==0)
        DataOutput <= 0;
    else
        if(enable==1)
            DataOutput<=DataInput;
end
end
endmodule
```

I created the new pipeline registers as well as instantiated their respective wires:

```
wire Flush_Jump_wire; //added
wire Flush_BranchNE_wire;
wire Flush_BranchEQ_wire;
wire Flush_RegDst_wire;
wire [2:0] Flush_ALUOp_wire;
wire Flush_ALUSrc_wire;
wire Flush_RegWrite_wire;
wire Flush_MemWrite_wire;
wire Flush_MemRead_wire;
wire Flush_MemToReg_wire;
wire Flush_Jal_wire;
wire ID_Flush_BranchNE_wire_EX; //added
wire ID_Flush_BranchEQ_wire_EX; //added
wire Flush_Jr_wire; //added
wire ID_Flush_Jump_wire_EX; //added
wire ID_Flush_RegWrite_wire_EX;
wire ID_Flush_MemWrite_wire_EX;
wire ID_Flush_MemRead_wire_EX;
wire ID_Flush_MemToReg_wire_EX;
wire ID_Flush_Jal_wire_EX;
wire [2:0] ALUOp_wire;
wire [3:0] ALUOperation_wire;
wire [4:0] WriteRegister_wire;
wire [1:0] ForwardA_wire;
wire [1:0] ForwardB_wire;
wire [31:0] ReadData1_wire;
wire [31:0] ReadData2_wire;
wire [31:0] ImmediateExtend_wire;
wire [31:0] PC_ImmediateExtend_wire;
wire [31:0] ALUResult_wire;
wire [31:0] ReadDataOut_wire;
wire [31:0] PC_wire;
wire [31:0] PC_4_wire;
wire [31:0] ReadData2OrImmediate_wire;
wire [31:0] Instruction_wire;
wire [31:0] Jump_PC_wire;
wire [31:0] MUX_FinalPC_wire;
wire [31:0] MUX_PC_Stall_wire;
wire [31:0] MUX_WriteData_wire;
wire [31:0] MUX_FinalWriteData_wire;
wire [4:0] MUX_WriteRegister_wire;
wire [31:0] MUX_Jump_wire;
wire [31:0] MUX_Jr_wire;
wire [31:0] MUX_Output_A_wire;
wire [31:0] MUX_Output_B_wire;
wire [31:0] Flush_Instruction_wire;

//Pipeline IF to ID
wire [31:0] IF_PC_4_wire_ID;
wire [31:0] IF_Instruction_wire_ID;

//Pipeline ID to EX
wire ID_Jump_wire_EX; //1
wire ID_Jal_wire_EX; //1
wire ID_RegDst_wire_EX; //1
wire ID_BranchNE_wire_EX; //1
wire ID_BranchEQ_wire_EX; //1
wire ID_ALUSrc_wire_EX;
wire ID_RegWrite_wire_EX;
wire ID_MemWrite_wire_EX;
wire ID_MemRead_wire_EX;
wire ID_MemToReg_wire_EX;
wire [2:0] ID_ALUOp_wire_EX;
wire [31:0] ID_PC_4_wire_EX;
wire [31:0] ID_ReadData1_wire_EX;
wire [31:0] ID_ReadData2_wire_EX;
wire [31:0] ID_Instruction_wire_EX;
wire [31:0] ID_ImmediateExtend_wire_EX;
//Pipeline Ex to to MEM
wire EX_Jal_wire_MEM; //1
wire EX_Jr_wire_MEM;
wire EX_Jump_wire_MEM;
wire EX_BranchNE_wire_MEM; //1
wire EX_BranchEQ_wire_MEM; //1
wire EX_MemToReg_wire_MEM;
wire EX_MemWrite_wire_MEM;
```

```

Pipeline
#(
    .N(143)
)
EX_Pipeline_MEM
(
    .clk(clk),
    .reset(reset),
    .enable(1),
    .DataInput({
        ID_ReadData1_wire_EX,
        ID_Flush_Jal_wire_EX,
        ID_PC_4_wire_EX,
        ID_Flush_BranchNE_wire_EX,//added
        ID_Flush_BranchEQ_wire_EX,//added
        Flush_Jr_wire,//added
        ID_Flush_Jump_wire_EX,//added
        ID_Flush_RegWrite_wire_EX,
        ID_Flush_MemWrite_wire_EX,
        ID_Flush_MemRead_wire_EX,
        ID_Flush_MemtoReg_wire_EX,
        Zero_wire,
        ALUResult_wire,
        MUX_Output_B_wire,
        WriteRegister_wire
    })),
    .DataOutput({
        EX_ReadData1_wire_MEM,
        EX_Jal_wire_MEM,
        EX_PC_4_wire_MEM,
        EX_BranchNE_wire_MEM, //1
        EX_BranchEQ_wire_MEM, //1
        EX_Jr_wire_MEM,
        EX_Jump_wire_MEM,
        EX_RegWrite_wire_MEM,
        EX_MemWrite_wire_MEM,
        EX_MemRead_wire_MEM,
        EX_MemtoReg_wire_MEM,
        EX_Zero_wire_MEM,
        EX_ALUResult_wire_MEM,
        EX_ReadData2_wire_MEM,
        EX_MUX_ForRTypeAndIType_wire_MEM
    })
);

Pipeline
#(
    .N(104)
)
MEM_Pipeline_WB
(
    .clk(clk),
    .reset(reset),
    .enable(1),
    .DataInput({
        EX_Jal_wire_MEM,
        EX_PC_4_wire_MEM,
        EX_RegWrite_wire_MEM,
        EX_MemtoReg_wire_MEM,
        ReadDataOut_wire,
        EX_ALUResult_wire_MEM,
        EX_MUX_ForRTypeAndIType_wire_MEM
    })),

```

I also had to change all of the previous modules' inputs and outputs in order to work with the new naming schema/system:

```

MUX_ForRTypeAndIType          //rt rd
(
    .Selector(ID_RegDst_wire_EX),
    .MUX_Data0(ID_Instruction_wire_Ex[20:16]),
    .MUX_Data1(ID_Instruction_wire_Ex[15:11]),
    .MUX_Output(MUX_WriteRegister_wire)
);

RegisterFile
Register_File
(
    .clk(clk),
    .reset(reset),
    .RegWrite(MEM_RegWrite_wire_WB),
    .WriteRegister(MEM_MUX_ForRTypeAndIType_wire_WB),
    .ReadRegister1(IF_Instruction_wire_ID[25:21]), //rs
    .ReadRegister2(IF_Instruction_wire_ID[20:16]), //rt
    .WriteData(MUX_FinalWriteData_wire),
    .ReadData1(ReadData1_wire),
    .ReadData2(ReadData2_wire)
);

SignExtend
SignExtendForConstants
(
    .DataInput(IF_Instruction_wire_ID[15:0]),
    .SignExtendOutput(ImmediateExtend_wire)
);

Multiplexer2to1
#(
    .N(32)
)
MUX_ForReadDataAndImmediate
(
    .Selector(ID_ALUSrc_wire_EX),
    .MUX_Data0(MUX_Output_B_wire),
    .MUX_Data1(ID_ImmediateExtend_wire_EX),
    .MUX_Output(ReadData2OrImmediate_wire)
);

ALUControl
ArithmeticLogicUnitControl
(
    .ALUOp(ID_ALUOp_wire_EX),
    .ALUFunction(ID_ImmediateExtend_wire_EX[5:0]),
    .ALUOperation(ALUOperation_wire),
    .Jr(Jr_wire)
);

ALU
ArithmeticLogicUnit
(
    .ALUOperation(ALUOperation_wire),
    .A(MUX_Output_A_wire),
    .B(ReadData2OrImmediate_wire),
    .Z(Z_wire),
    .S(S_wire),
    .O(O_wire),
    .C(C_wire)
);

```

For the forwarding unit, I created a new register and added the combinational algorithm proposed in the course's presentation:

```

input EX_RegWrite_wire_MEM,
input MEM_RegWrite_wire_WB,
input [N-1:0] EX_RegisterRd_wire_MEM,
input [N-1:0] ID_RegisterRs_wire_EX,
input [N-1:0] ID_RegisterRt_wire_EX,
input [N-1:0] MEM_RegisterRd_wire_WB,

output reg [1:0] ForwardA,
output reg [1:0] ForwardB
);

always@(EX_RegWrite_wire_MEM,
        MEM_RegWrite_wire_WB,
        EX_RegisterRd_wire_MEM,
        ID_RegisterRs_wire_EX,
        ID_RegisterRt_wire_EX,
        MEM_RegisterRd_wire_WB)begin

    if(EX_RegWrite_wire_MEM == 0 &&
        EX_RegisterRd_wire_MEM != 0 &&
        EX_RegisterRd_wire_MEM == ID_RegisterRs_wire_EX)
        ForwardA = 2'b10;
    else
        if(MEM_RegWrite_wire_WB == 0 &&
            MEM_RegisterRd_wire_WB != 0 &&
            EX_RegisterRd_wire_MEM != ID_RegisterRs_wire_EX &&
            MEM_RegisterRd_wire_WB == ID_RegisterRs_wire_EX)
            ForwardA = 2'b01;
        else
            ForwardA = 2'b00;
    if(EX_RegWrite_wire_MEM == 0 &&
        EX_RegisterRd_wire_MEM != 0 &&
        EX_RegisterRd_wire_MEM == ID_RegisterRt_wire_EX)
        ForwardB = 2'b10;
    else
        if(MEM_RegWrite_wire_WB == 0 &&
            MEM_RegisterRd_wire_WB != 0 &&
            EX_RegisterRd_wire_MEM != ID_RegisterRt_wire_EX &&
            MEM_RegisterRd_wire_WB == ID_RegisterRt_wire_EX)
            ForwardB = 2'b01;
        else
            ForwardB = 2'b00;

end

endmodule

ForwardingUnit
(
    .ID_RegisterRs_wire_EX(ID_Instruction_wire_Ex[25:21]),
    .ID_RegisterRt_wire_EX(ID_Instruction_wire_Ex[20:16]),
    .EX_RegisterRd_wire_MEM(EX_MUX_ForRTypeAndIType_wire_MEM),
    .EX_RegWrite_wire_MEM(EX_RegWrite_wire_MEM),
    .MEM_RegisterRd_wire_WB(MEM_MUX_ForRTypeAndIType_wire_WB),
    .MEM_RegWrite_wire_WB(MEM_RegWrite_wire_WB),
    .ForwardA(ForwardA_wire),
    .ForwardB(ForwardB_wire)
);

Multiplexer3to1
#(
    .N(32)
)
MUX_ForA
(
    .Selector(ForwardA_wire),
    .MUX_Data0(ID_ReadData1_wire_EX),
    .MUX_Data1(MUX_FinalWriteData_wire),
    .MUX_Data2(EX_ALUResult_wire_MEM),

    .MUX_Output(MUX_Output_A_wire)
);

Multiplexer3to1
#(
    .N(32)
)
MUX_ForB
(
    .Selector(ForwardB_wire),
    .MUX_Data0(ID_ReadData2_wire_EX),
    .MUX_Data1(MUX_FinalWriteData_wire),
    .MUX_Data2(EX_ALUResult_wire_MEM),

    .MUX_Output(MUX_Output_B_wire)
);

```

For hazard detection, I created a new register type where the ins and outs would depend on the

```
module HazardUnit
#(
    parameter N=5
)
(
    input ID_MemRead_wire_EX,
    input [N-1:0] ID_RegisterRt_wire_EX,
    input [N-1:0] IF_RegisterRs_wire_ID,
    input [N-1:0] IF_RegisterRt_wire_ID,

    output reg Flush_wire,
    output reg IF_Enable_wire_ID,
    output reg Stall_wire
);

    always@(ID_MemRead_wire_EX,
            ID_RegisterRt_wire_EX,
            IF_RegisterRs_wire_ID,
            IF_RegisterRt_wire_ID)
    begin
        if (ID_MemRead_wire_EX &&
            (ID_RegisterRt_wire_EX ==
             IF_RegisterRs_wire_ID || ID_RegisterRt_wire_EX ==
             IF_RegisterRt_wire_ID))
            begin
                Flush_wire = 1;
                IF_Enable_wire_ID = 0;
                Stall_wire = 1;
            end
        else
            begin
                Flush_wire = 0;
                IF_Enable_wire_ID = 1;
                Stall_wire = 0;
            end
        end
    end
endmodule
```


For both of the new HDU/FWU, I had to create a and update new mux types that would either reset a signal after ID or to just pass 0 as a predefined parameter (flush or stall the stage) according to the instruction scenario – for the branch prediction status, I would always assume the branch would not be taken so that a flush mux would then pass a predefined 0 signal to the IF/ID out pipe in order to “cancel” the rest of the conflicting/not needed instruction:

```
module Multiplexer3to1
#
(
    parameter N=32
)
(
    input [1:0] Selector,
    input [N-1:0] MUX_Data0,
    input [N-1:0] MUX_Data1,
    input [N-1:0] MUX_Data2,
    output reg [N-1:0] MUX_Output
);

    always@(Selector,MUX_Data0,MUX_Data1,MUX_Data2)
    begin
        case (Selector)
            2'b00: MUX_Output <= MUX_Data0;
            2'b01: MUX_Output <= MUX_Data1;
            2'b10: MUX_Output <= MUX_Data2;
            default: MUX_Output <= 'b0;
        endcase
    end
endmodule
```

```

Hazard
(
    .ID_MemRead_wire_EX(ID_MemRead_wire_EX),
    .ID_RegisterRt_wire_EX(ID_Instruction_wire_EX[20:16]),
    .IF_RegisterRs_wire_ID(IF_Instruction_wire_ID[25:21]),
    .IF_RegisterRt_wire_ID(IF_Instruction_wire_ID[20:16]),
    .Flush_wire(Flush_wire),
    .IF_Enable_wire_ID(IF_Enable_wire_ID),
    .Stall_wire(Stall_wire)
);

Multiplexer2to1
#(
    .N(32)
)
MUX_Stall
(
    .Selector(Stall_wire),
    .MUX_Data0(MUX_FinalPC_wire),
    .MUX_Data1(PC_wire),
    .MUX_Output(MUX_PC_Stall_wire)
);

Multiplexer2to1
MUX_IF_Flush_ID
(
    .Selector(PCtoBranch_wire | Jump_wire | Jr_wire),
    .MUX_Data0(Instruction_wire),
    .MUX_Data1(0),
    .MUX_Output(Flush_Instruction_wire)
);

Multiplexer2to1
#(
    .N(12)
)
MUX_ID_Flush_EX
(
    .Selector(Flush_wire | PCtoBranch_wire | EX_Jump_wire_MEM |
EX_Jr_wire_MEM),
    .MUX_Data0({
        Jal_wire,
        Jump_wire, //1
        BranchNE_wire, //1
        BranchEQ_wire, //1
        RegDst_wire, //1
        ALUOp_wire, //3
        ALUSrc_wire, //1
        RegWrite_wire, //1
        MemWrite_wire, //1
        MemRead_wire, //1
        MemToReg_wire, //1
    },
    .MUX_Data1(0),
    .MUX_Output({
        Flush_Jal_wire,
        Flush_Jump_wire, //added
        Flush_BranchNE_wire,
        Flush_BranchEQ_wire,
        Flush_RegDst_wire,

        Flush_ALUOp_wire,

        Flush_ALUSrc_wire,

        Flush_RegWrite_wire,

        Flush_MemWrite_wire,


        Flush_MemRead_wire,

        Flush_MemToReg_wire
    }
);

```

Test and debugging:

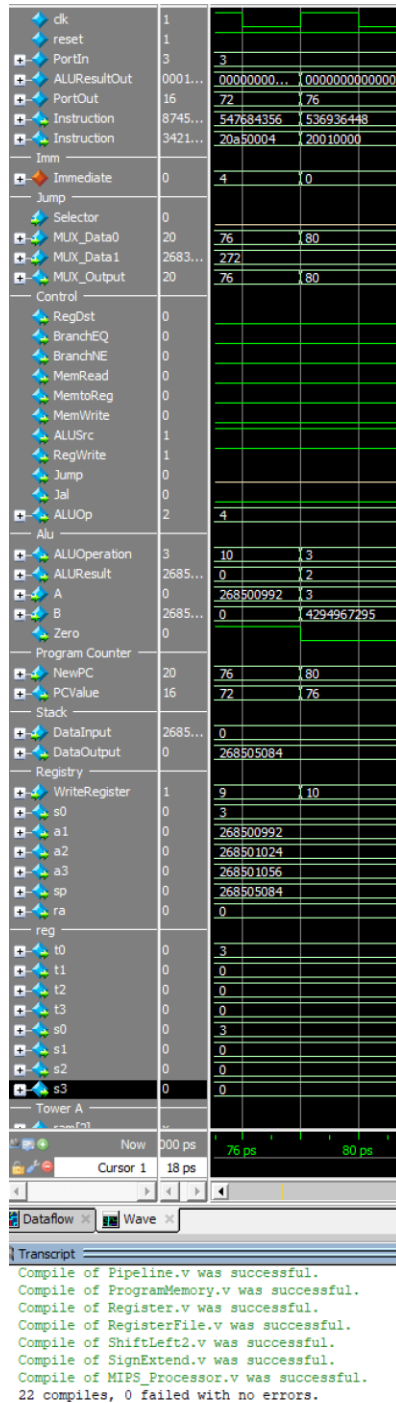For simulation on ModelSim, I first created a wave viewer/map where I would be adding new registers ins and outs from time to time according to my needs for debugging each stage:



Instruction tests:

I created a set of programs that would test each of the initially implemented instruction at its most basic operation level. All of them are included in the archive.

pipeTest (test with nop's stalling)

```
.text
    addi $t0, $zero, 5
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    add $t1, $t0, $zero
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    addi $t1, $t1, 2
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    addi $t2, $t1, 3
    addi $t3, $t3, 0x1001
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    sll $t3, $t3, 16
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    sw $t2, 0($t3)
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    add $s0, $t2, $t1
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    sub $s1, $s0, $t3
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    lw $t2, 0($t3)
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    addi $s2, $t2, -2
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    or $s2, $s2, $t4
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    add $zero, $zero, $zero
    sll $s7, $s2, 2
exit:
```

pipefwTest (test no nop)

```
.text
    addi $t0, $zero, 5
    add $t1, $t0, $zero
    addi $t1, $t1, 2
    addi $t2, $t1, 3
    addi $t3, $t3, 0x1001
    sll $t3, $t3, 16
    sw $t2, 0($t3)
    add $s0, $t2, $t1
    sub $s1, $s0, $t3
    lw $t2, 0($t3)
    addi $s2, $t2, -2
    or $s2, $s2, $t4
    sll $s7, $s2, 2
exit:
```

Bne (test flush after ID on conflicting instruction)

```
#BNE test
addi $t0, $zero, 2
bne $t0,$zero bneWORKS
addi $t0, $zero, 1 #si t1 llega a ser 1, no hizo branch
bneWORKS:
```

Beq (test flush)

```
#beq test
addi $t1, $zero, 0
beq $t1,$zero beqWORKS
addi $t1, $zero, 1 #si t1 llega a ser 1, no hizo branch
beqWORKS:
```

lswTest


```
#lw/sw test
.text
    addi $s1, $zero, 0x1001
    sll $s1, $s1, 16
    addi $t0, $zero, 5
    sw $t0, 0($s1)
    lw $t1, 0($s1)
```

J types and Hanoi:

Even though the above test did work/pass, unfortunately, and here's where I failed, I never seemed to either fix or even understand the J type instructions through a pipeline approach; I couldn't seem to figure the Datapath that a jump address would have to go through/by in order to go to the stage it is needed at the precise cycle it is needed. And yes, I tried using nop's...

jTest
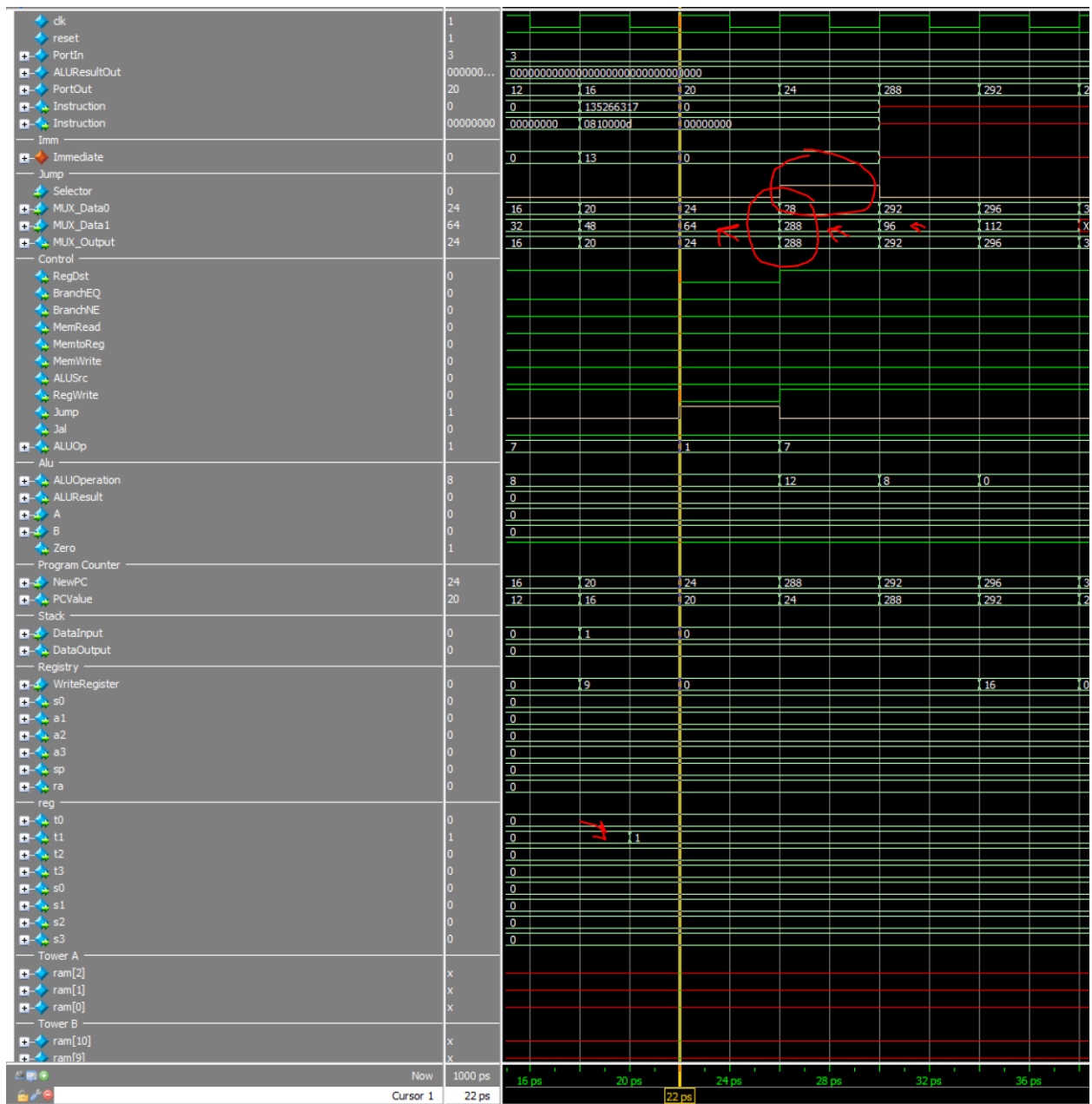
```
#addi $sp,$zero,268505084
# j test
addi $t1, $zero, 1
j Exit
addi $t2, $zero, 2
Exit:
addi $t3, $zero, 3
```




jrTest

```


|#JR test
addi $t0, $zero, 1
jal TEST
addi $t0, $zero, 3
j Exit
TEST:
addi $t0, $zero, 2
jr $ra
Exit:

```

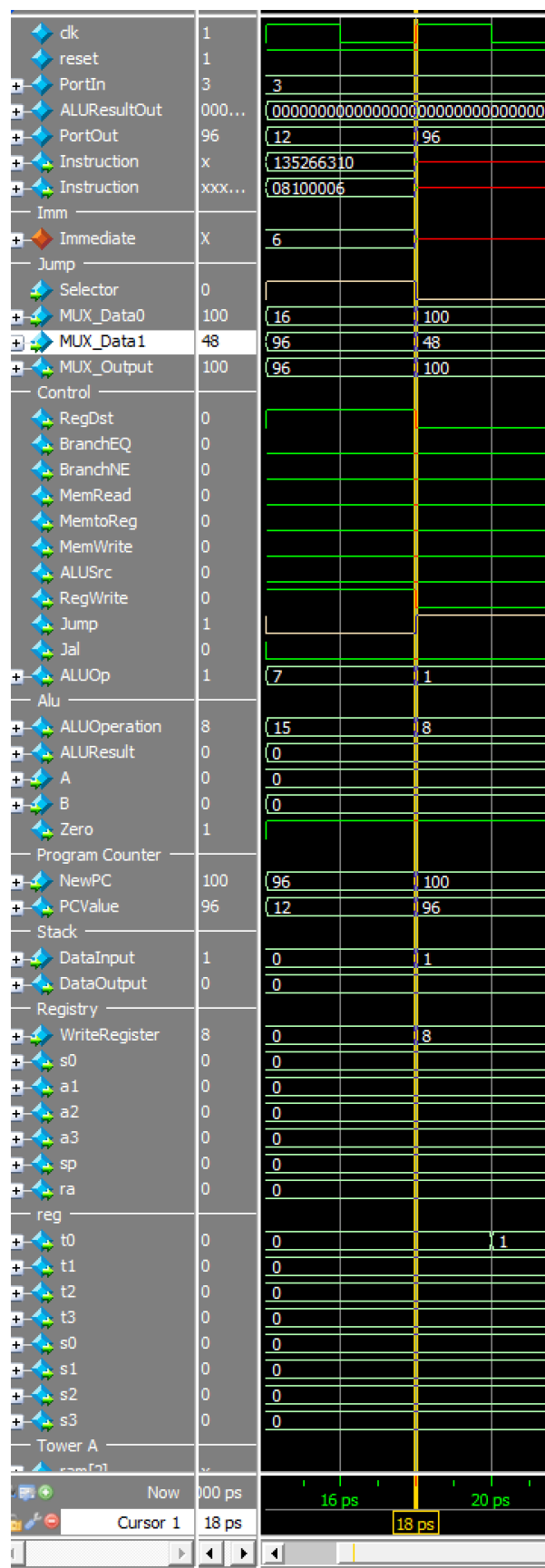


Hanoi ("hanoiTest")

For Hanoi, as the j type instructions were broken the moment I tried to pipeline my original approach, the program did not work right at the moment where the first Jal is used: it calls the Hanoi Tower recursively after linking its current address, but there were lots of different problems – sometimes it even wrote the \$ra data on a random register like \$so. In this case, I also tried to nop the hell out of the original program and no, neither did work:

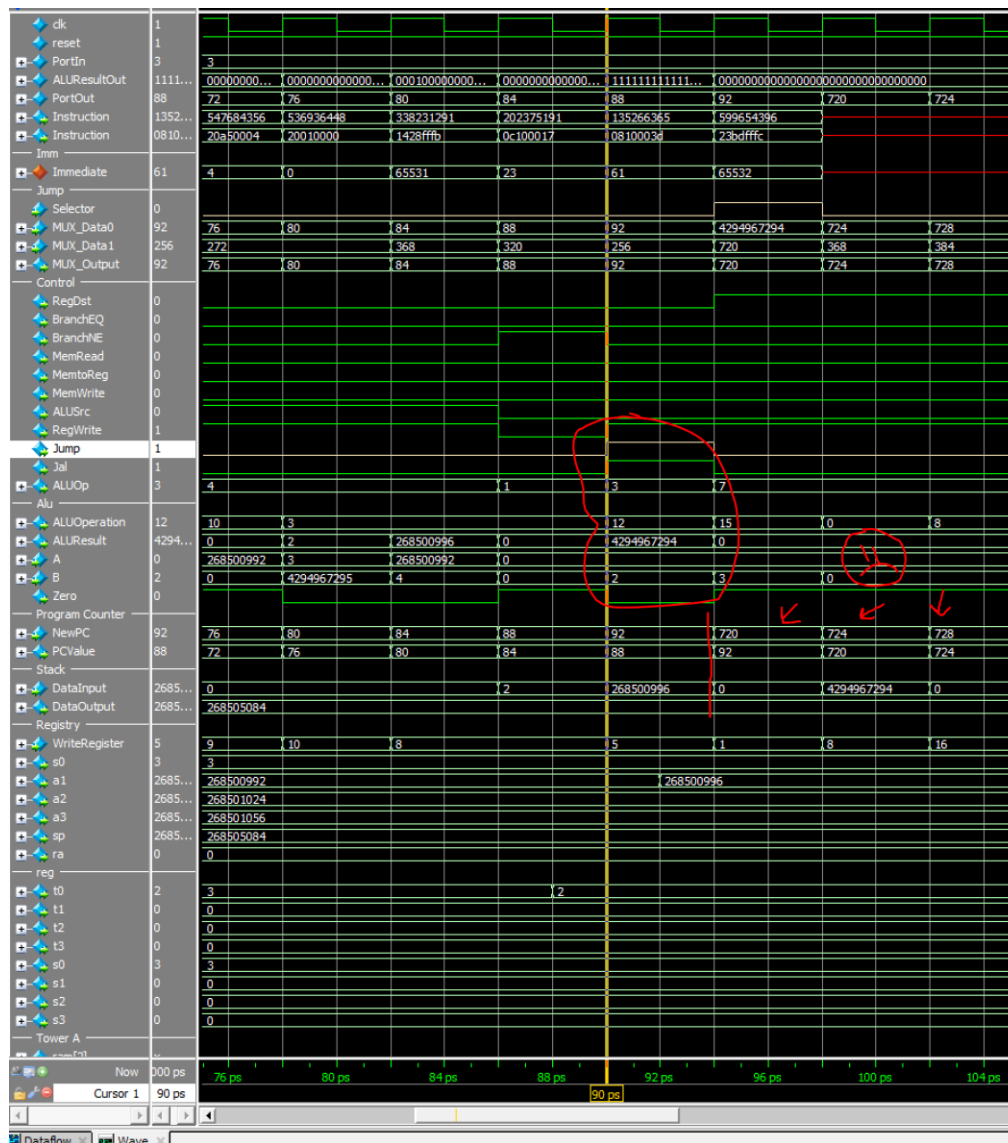

3. RTL Diagram

 


4. Clock rate and CPU comparison:


Single Cycled and Pipelined

Slow 1200mV OC Model Fmax Summary				
<<Filter>>				
	Fmax	Restricted Fmax	Clock Name	Note
1	87.17 MHz	87.17 MHz	clk	

Slow 1200mV OC Model Fmax Summary				
<<Filter>>				
	Fmax	Restricted Fmax	Clock Name	Note
1	44.5 MHz	44.5 MHz	clk	

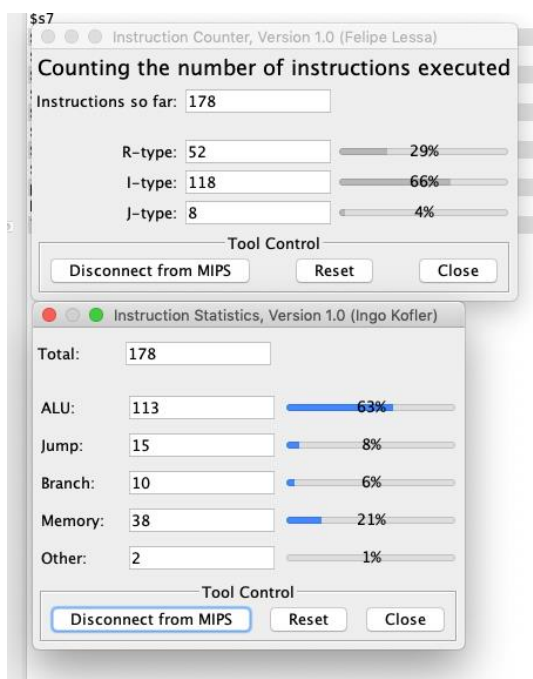

5. Flow diagram and description:

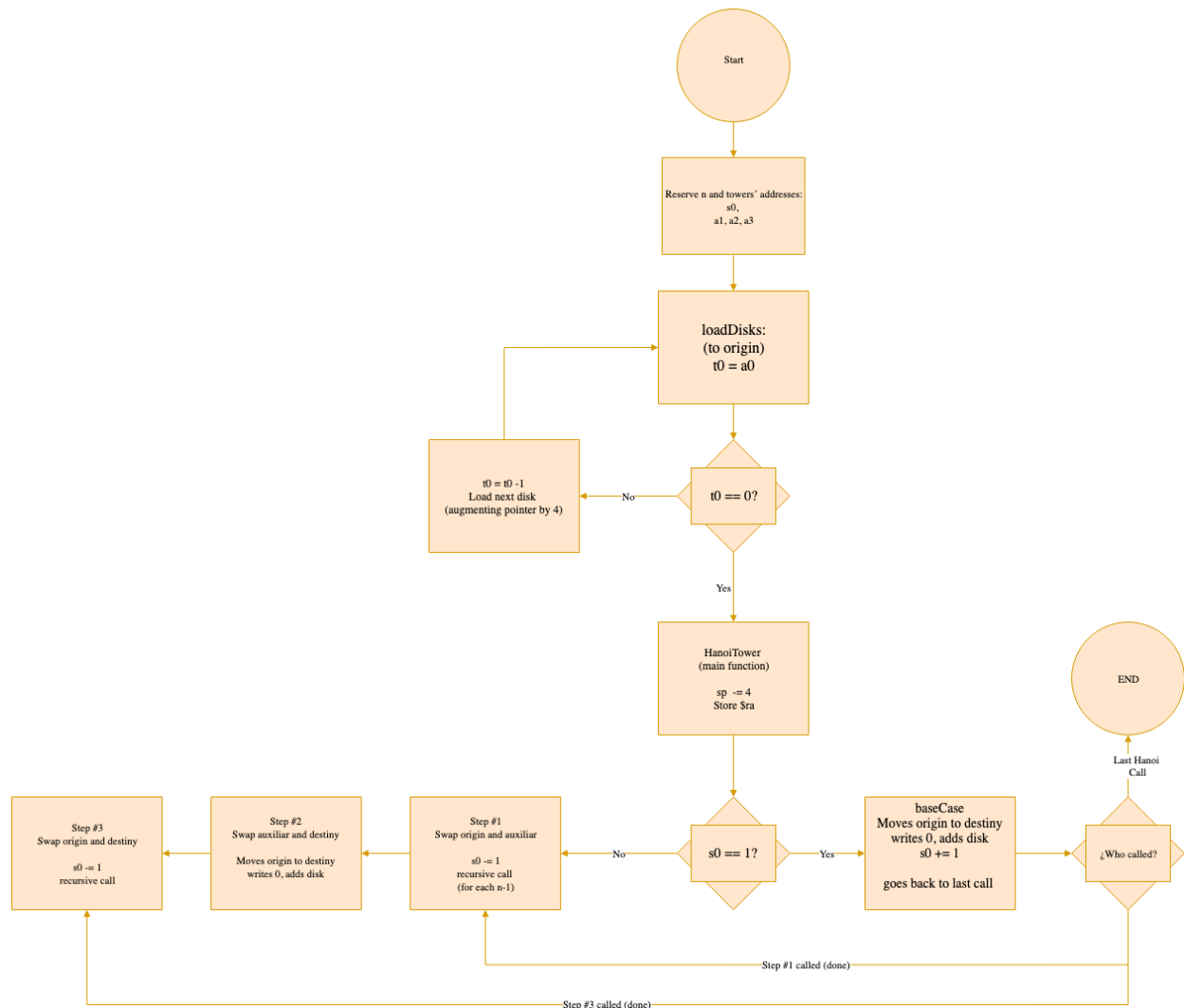

Flow description:

My algorithm would begin by associating each of the addresses to each of its respective tower as well as register. We'd also always have n stored in $s0$, even though such variable is inputed by the user beforehand.

The loadDisks function or subroutine would then begin to load each and every disk onto its respective space or place on tower A/origin tower until the amount of disks are complete. And then it would proceed to call the HanoiTower function for the first time, which would initially allocate the memory necessary to store the ra registry onto the top stack position.

The function would first try to validate whether the amount of disks is or isn't 1 in order to jump to the base case (which would move the respective tower to its according position) or to the internal function steps (which would swap the pointers or addresses on each of the towers accordingly in order to follow the algorithm described on the assignment).

The process would loop in and out of the steps, unwinding and then rewinding when its ready to swap the disks to their respective next tower, step by step, all by switching the auxiliary tower accordingly. Once the algorithms takes us to the last step or to the top of the rewinding process, it would put the last disk onto its final place and finally it would restore the size of the sp as well as s0 to finally be done with the process.

9 – Files

Check the included archive, where the top and rest of the v files, pdf architecture and flow diagrams are also included.